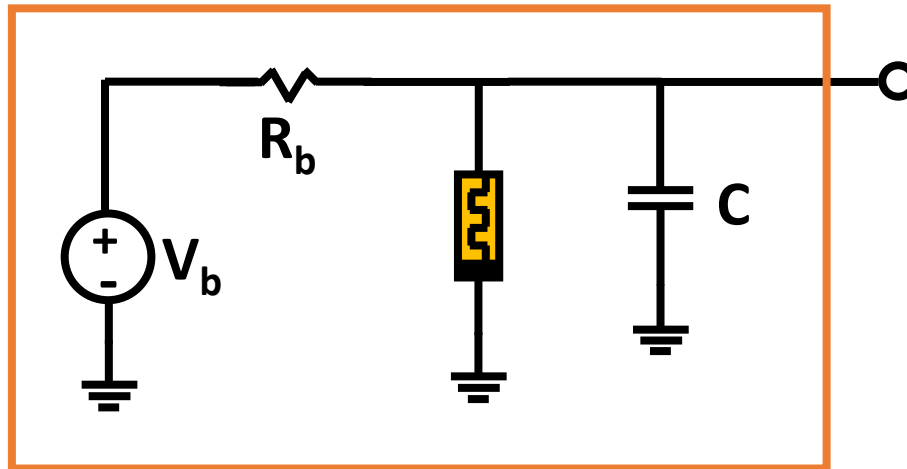


SINGLE CELL



Equations

$$C \frac{dV_c}{dt} = \frac{V_b - V_c}{R_b} - G(T) \cdot V_c$$

$$C_{th} \frac{dT}{dt} = V_c^2 \cdot G(T) - (T - T_0) \cdot g_{th}$$

$$G(T) = g_0 \exp(-g_1/T)$$


Parameters

```
g0=5e-3; g1=1700;  
Cth=1e-14; gth=1/1.5e6; T0=300;  
Vb=1.1; Rb=1e3; C=10e-9;
```


Initial conditions

```
T_init = 300; Vc_init = 0.001;
```

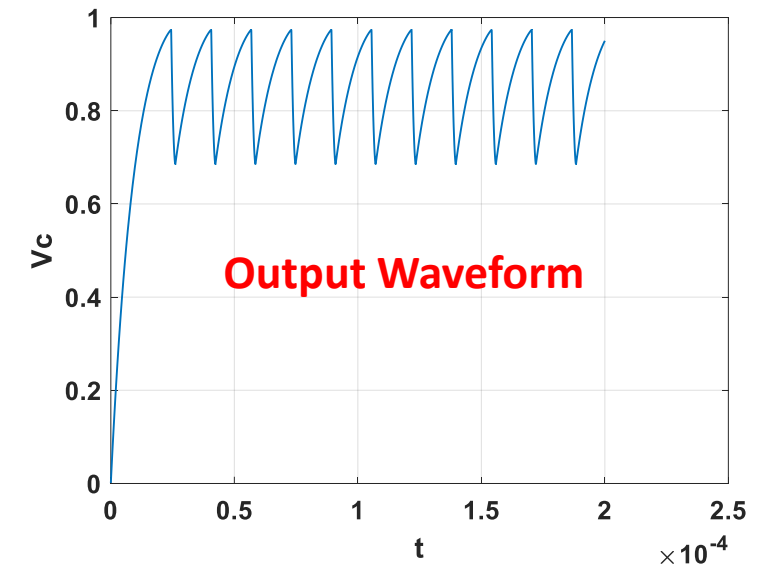Solve the equations Matlab/Python
Try to obtain the same output waveform!



SINGLE CELL with Rs

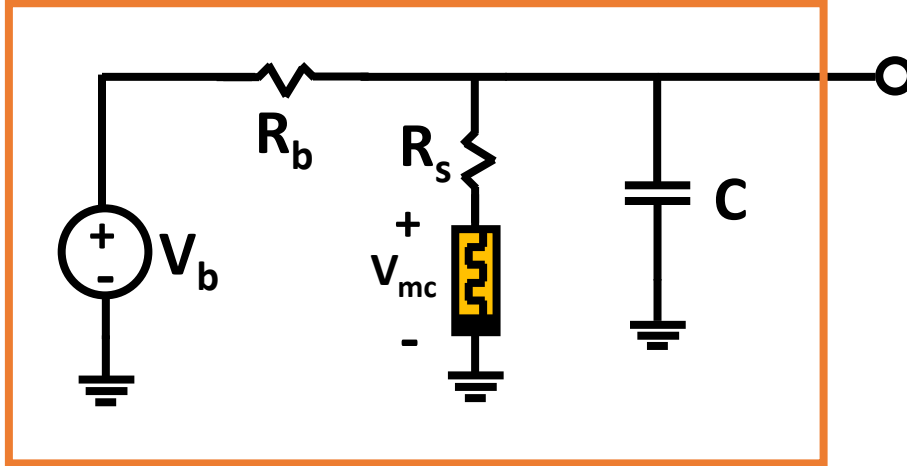

Parameters

```
g0=5e-3; g1=1700;  
Cth=1e-14; gth=1/1.5e6; T0=300;  
Vb=1.1; Rb=1e3; C=10e-9;  
Rs=200;
```

Initial conditions

```
T_init = 300; Vc_init = 0.001;
```

Solve the equations Matlab/Python
Try to obtain the same output waveform!


Equations

$$C \frac{dV_c}{dt} = \frac{V_b - V_c}{R_b} - G(T) \cdot V_m$$


$$C_{th} \frac{dT}{dt} = V_{mc}^2 \cdot G(T) - (T - T_0) \cdot g_{th}$$

$$G(T) = g_0 \exp(-g_1/T)$$

$$V_{mc} = \frac{V_c}{1 + G(T) \cdot R_s}$$

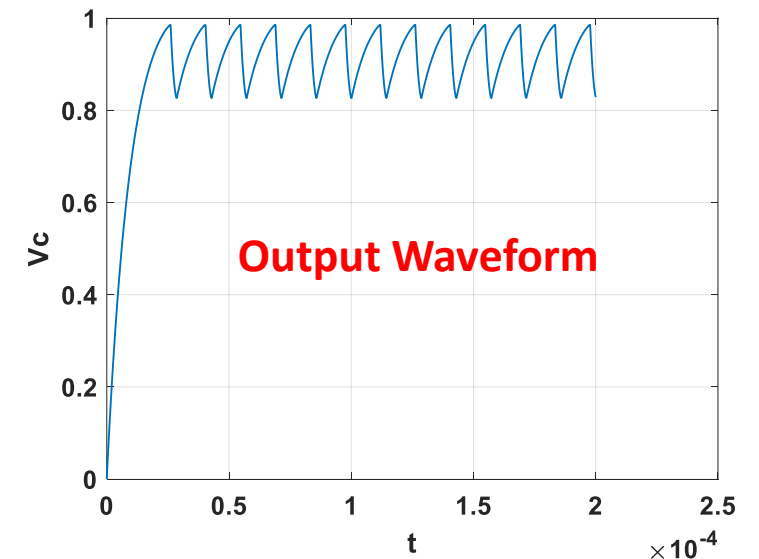

DC I-V characteristics

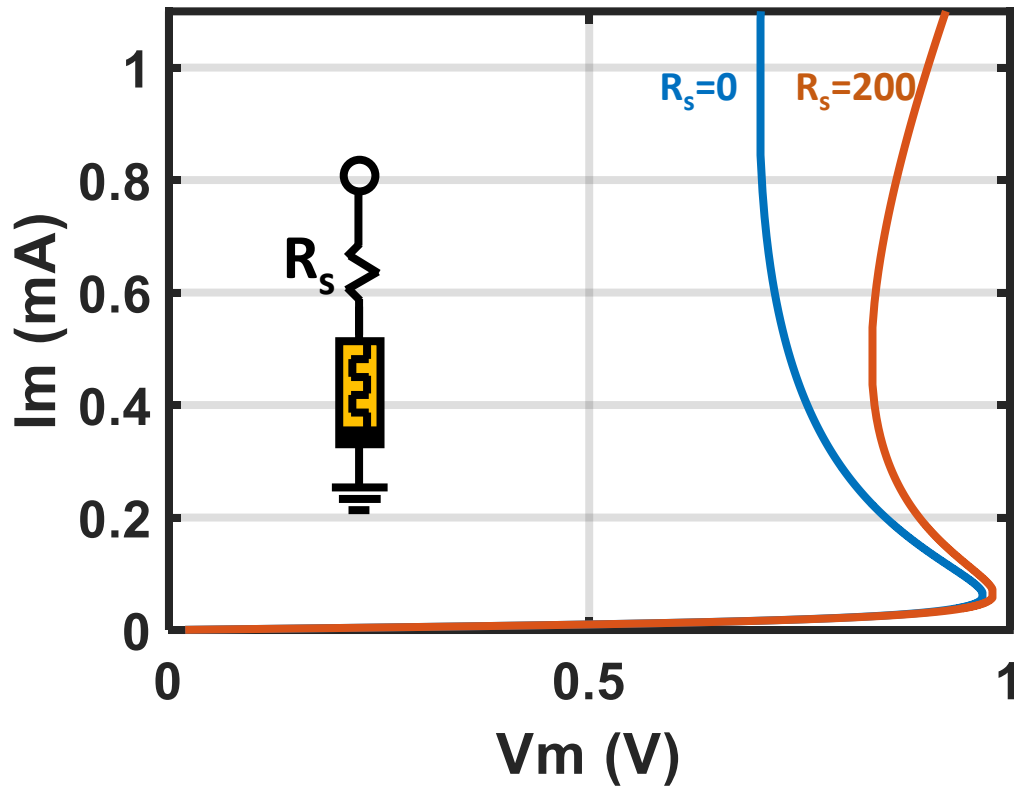

Define T as a parameter to be swept

```
T = 300.01 : 0.01 : 7000;
```


Set $\rightarrow \frac{dT}{dt} = 0$

```
vmc = sqrt(gth*(T-T0)/G(T));
```

```
im = vmc*G(T);
```

```
vm = vmc*(1+Rs*G(T));
```

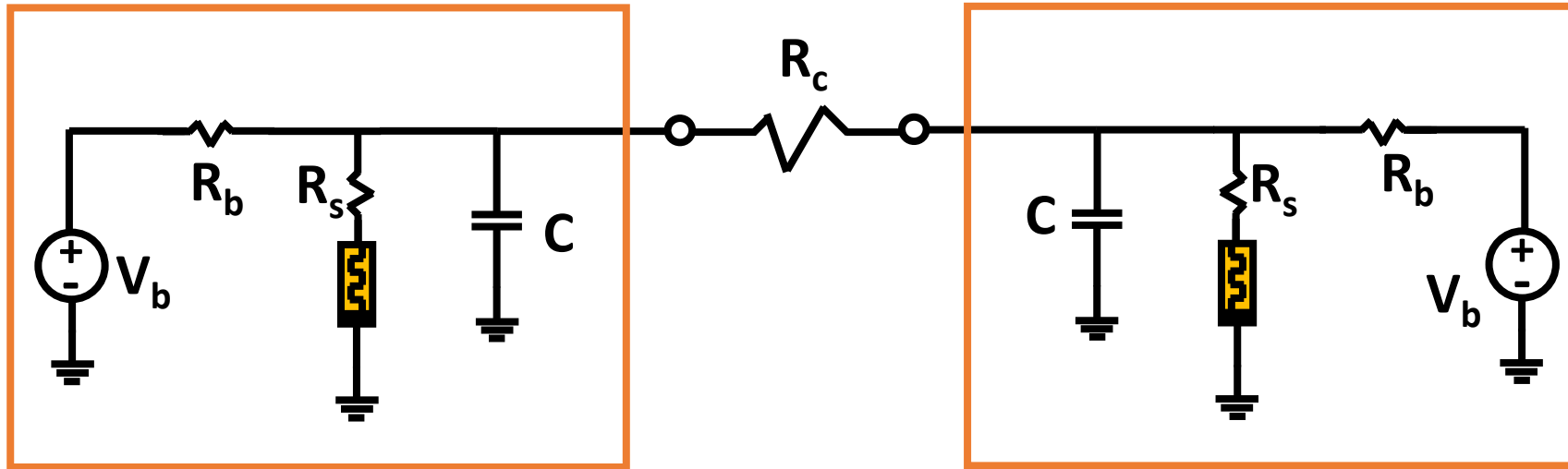Try to obtain the same DC I-V characteristics yourself!



$$C \frac{dV_{c1}}{dt} = \frac{V_b - V_{c1}}{R_b} - G(T) \cdot V_{mc1} - (V_{c1} - V_{c2})/R_c$$

$$C \frac{dV_{c2}}{dt} = \dots$$

Try to write down the equations and simulate if possible!